

## 0.1 Exercise 1: Design and Implementation of NOT Gates Using Transistors

### High-Level and Low-Level Input Voltages

The high-level input voltage ( $V_{IH}$ ) is the minimum input voltage that is considered as high, while the low-level input voltage ( $V_{IL}$ ) is the maximum input voltage that is considered as low.

### High-Level and Low-Level Output Voltages

The high-level output voltage ( $V_{OH}$ ) is the minimum output voltage that the circuit provides as a high, while the low-level output voltage ( $V_{OL}$ ) is the maximum output voltage that the circuit provides as a low.

### Noise Margin

The high noise margin ( $NM_H$ ) is the gap between the high-level input voltage and the high-level output voltage, while the low noise margin ( $NM_L$ ) is the gap between the low-level output voltage and the low-level input voltage.

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

### Propagation Delays

For this assignment's measures, when the input changes from low to high and the output from high to low, the high-to-low propagation delay is considered as the time between the moment in which the input voltage reaches the 90% of its maximum high value, until the moment in which the output voltage reaches the 10% of its maximum high value.

$$t_{pHL} = t_{10\%V_{maxO}} - t_{90\%V_{maxI}}$$

In the case in which the input goes from high to low and the output from low to high, the low-to-high propagation delay is considered as the time between the moment in which the input voltage reaches the 10% of its maximum high value, until the moment in which the output voltage reaches the 90% of its maximum high value.

$$t_{pLH} = t_{90\%V_{maxO}} - t_{10\%V_{maxI}}$$

## Transition Times

The high-to-low transition time or fall time ( $t_f$ ) is the time that it takes the output voltage to go from its high maximum value to its low minimum value, while the low-to-high transition time or rise time ( $t_r$ ) is the time that it takes for it to change from its low minimum value to its high maximum value.

## Maximum Output Current

### 0.1.1 Using a BJT NPN 337 Transistor

#### Without Load Connected to the Output

$$\begin{aligned}V_{IH} &= 0,9V \\V_{IL} &= 0,5V \\V_{OH} &= 4,96V \\V_{OL} &= 100mV\end{aligned}$$

$$\begin{aligned}NM_H &= 4,06V \\NM_L &= 0,4V\end{aligned}$$

$$\begin{aligned}t_{pHL} &= 87ns \\t_{pLH} &= 2,94\mu s\end{aligned}$$

$$\begin{aligned}t_f &= 69,5ns \\t_r &= 505ns\end{aligned}$$

$$MaximumOutputCurrent =$$

#### With a 1nF Capacitor Connected to the Output

### 0.1.2 Using a BJT PNP 327 Transistor

#### Without Load Connected to the Output

$$\begin{aligned}V_{IH} &= 4,5V \\V_{IL} &= 4,2V \\V_{OH} &= 4,77 \\V_{OL} &= 50mV\end{aligned}$$

$$\begin{aligned}NM_H &= 0,27V \\NM_L &= 4,15V\end{aligned}$$

$$\begin{aligned}t_{pHL} &= 2,72\mu s \\t_{pLH} &= 73ns\end{aligned}$$

$$t_f = 575ns$$

$$t_r = 83ns$$

*MaximumOutputCurrent* =

**With a  $1nF$  Capacitor Connected to the Output**