

# 1 Exercise 8

In this section we will explain how we developed the PCB that made the sensor HC-SR04 work using only digital electronics.

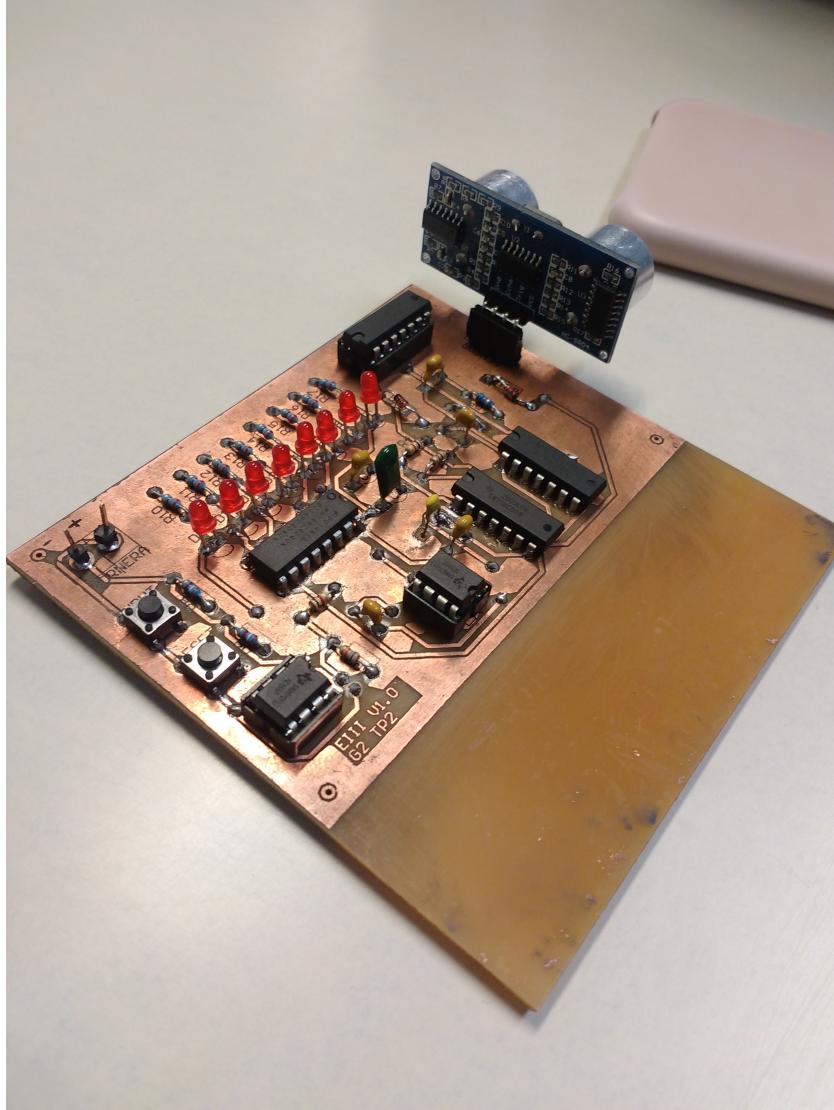


Figure 1: PCB

First of all we have to explain how that sensor works.

## 1.1 Sensor Operation

This sensor has 4 pins, 2 for supply voltage (VCC and GND), and another pair for control, these are 'Trig' and 'Echo'. The operation of this sensor is pretty simple, you have to send a pulse of time greater than  $10\mu S$  and after some time, it will return into pin Echo, a response pulse of duration that we will call  $T$ . If we find a method to measure the time  $T$ , we can calculate the distance measured with the following formula.

$$Distance = \frac{T}{58}$$

Its important to know that the time  $T$  has to be in units of  $\mu S$  for the formula to work properly, and  $Distance$  is in centimeters.

A diagram of this can be found in Figure 2

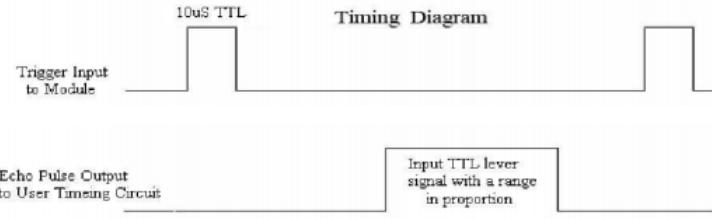


Figure 2: Sensor Input and output

## 1.2 Components used for this Printed Circuit Board

For this development we utilized the following Integrated Circuits and components:

- 74HC4040 Counter
- 74HC74 D-type flip-flop
- Two 74HC00 NAND gates
- Two NE555 Precision Timers
- Seven Capacitors
- Sixteen Resistors
- Two Diodes
- Eight Light Emitting Diodes

The disposition of this elements in the PCB will be explained as we understand how we made this work.

## 1.3 PCB Operation

To make this happen, we develop this board that roughly operates as shown in Figure 3

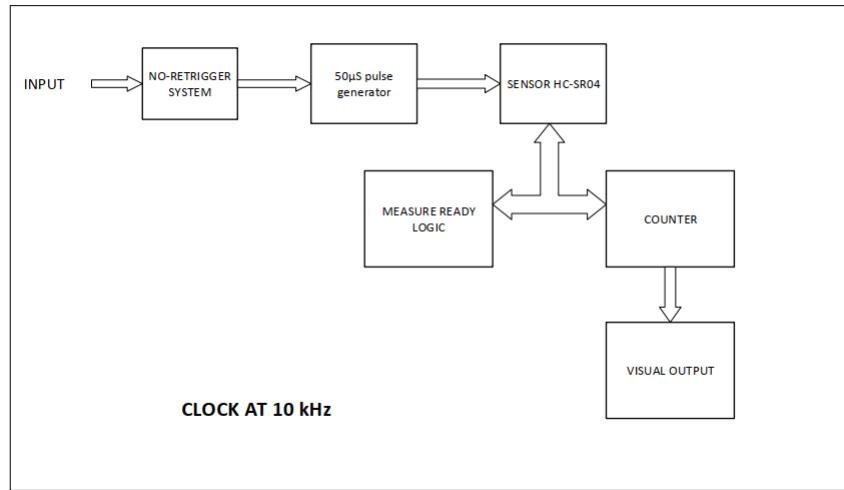


Figure 3: PCB diagram

First, we have a No-Retrigger System (NRS) that filters all the retrigged pulses we have because of buttons, that can make our board function in an unapropiate way. Then we generate a  $50\mu S$  pulse with the pulse generator, to send to the Trig pin of the sensor. Once we have the response of the sensor, we connect the Echo pin with the counter and the measure ready logic. And finally, we plug a visual output to the counter to see the measurement we have made. Every module seen on this diagram, is powered by a  $10kHz$  clock.

### 1.3.1 No-Retigger System operation

This system is powered by a 74HC74 D-type flip flop that with the proper connections we've changed it to an asynchronous SR Flip-Flop(SRFF). To make this, we connected the SRFF pins as follows:

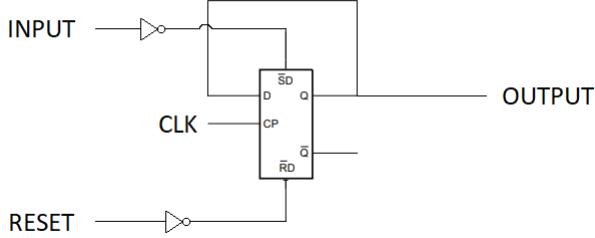


Figure 4: No-Retigger System Connections

By making this connections we made a feedback with the Q and D pins so by every positive-edge clock Q is maintained to its previous value, unless RESET is on. So, summarizing, by connecting the INPUT pin to the input button, and the RESET pin to the reset button, we've created a No-Retigger System for our board.

### 1.3.2 50 Microseconds Pulse Generator

Making this pulse generator was a challenge, but we achieved it by creating two submodules into the  $50\mu S$  Pulse Generator Module, these are the differentiator circuit, and the pulse generator circuit. Tough the Differentiator Circuit is placed before the Pulse Generator Circuit (PGC), we will explain first the PGC to better understand the utility of the Differentiator.

**Pulse Generator Circuit** To power this pulse generator we've used a NE555 Precision Timer, that by connecting it as shown in Figure 5, we have made a Pulse generator of the timme we wanted.

The formula to obtain the Pulse time at the output is the following

$$T = \ln(3)C3.R2$$

But there is a problem, this pulse generator only works if the input pulse time is less than the time calculated on the previous formula. So if we have a pulse generated by a human that is oviously greater than  $50\mu S$  we need a way to make this still work. So here is were the Differentiator Circuit comes to help.

**Differentiator Circuit** This circuit basically differentiates an input, for us, this means that whenever a pulse its made, a set of dirac's deltas comes out of the circuit, one positive, and another negative. If we define  $\tau$  as

$$\tau = RC$$

and we choose the apropiate values to the resistor and capacitor to make  $5\tau \leq 50\mu S$  we can have a really good differentiator circuit that for every input pulse, it creates an output of less than  $50\mu S$ , and we can make work our Pulse Generator.

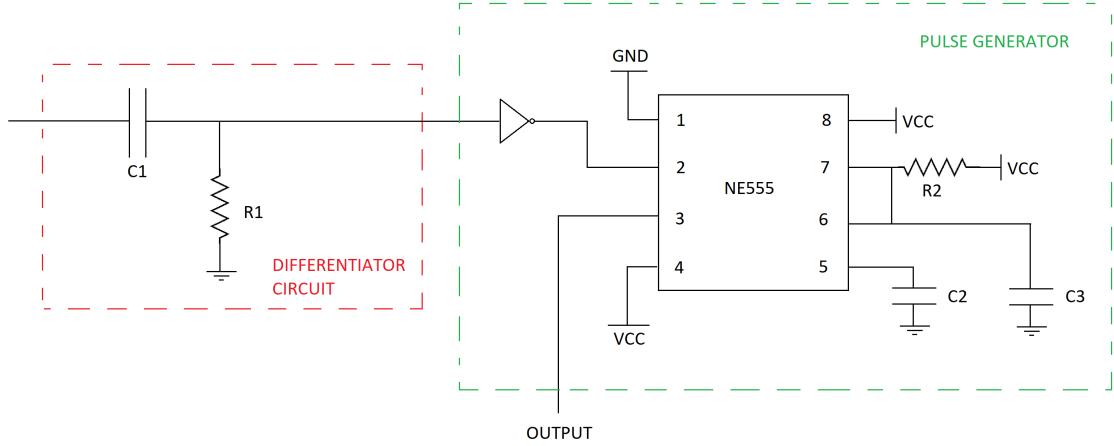


Figure 5: Pulse Generator

### 1.3.3 Measure Ready Logic

The measure ready logic is powered by a 74HC74 D-type flip flop used equally as the No-Retrigger System, and a differentiator circuit almost as equal as the Pulse generator differentiator circuit. But it has one little difference, the 74HC74 is very sensitive to negative voltage, and it can stop working properly according to its datasheet, so we had to add a little protection to erase the negative delta provided by the differentiator circuit. So the circuit became as shown in the Figure 6

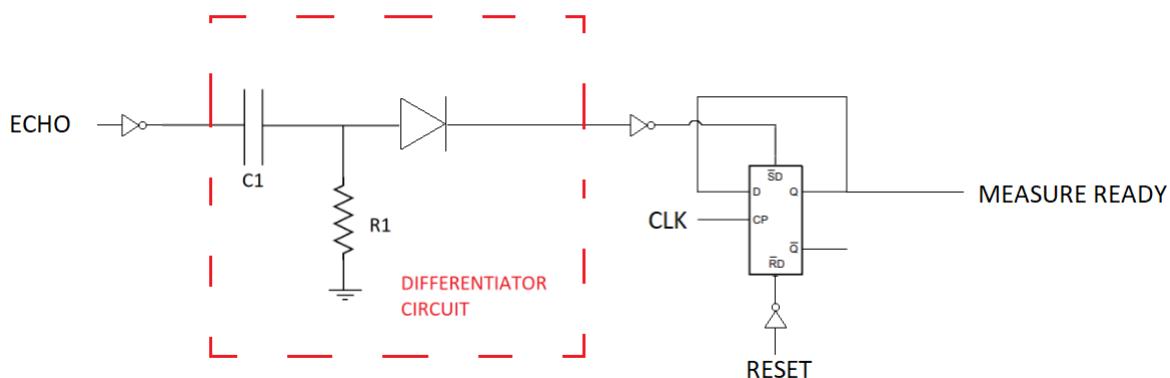


Figure 6: Measure Ready Logic

### 1.3.4 Counter

This circuit was relatively easy since we used a 74HC4040 Counter that was really intuitive to use, it was connected as shown in Figure 7

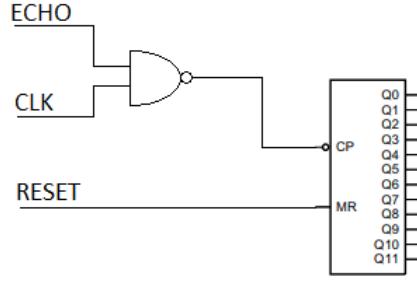


Figure 7: Counter

We implemented the NAND before the CP pin to count only when the Echo is on, and when it becomes off, the counter will stop counting.

### 1.3.5 Clock

The clock was performed also with a NE555 and by following the equation

$$T = \frac{1}{(R1 + 2.R2).C3}$$

we made a clock of the period needed. However, due to the resistor and capacitor values we had on the university, we only achieved a  $T$  of roughly of  $80\mu S$  instead of the  $100\mu S$  we wanted. Since it made no such big difference, we left it that way.


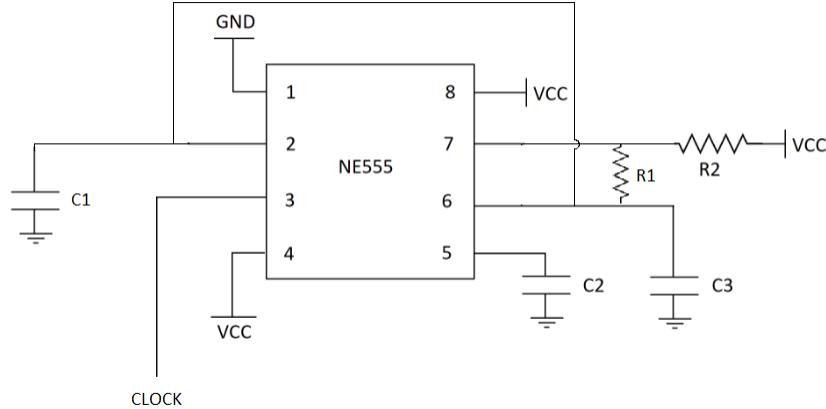


Figure 8: Clock

**Visual Output** Finally for this module, we decided to insert a simple array of LEDs displaying in binary code the measurement made by the sensor.
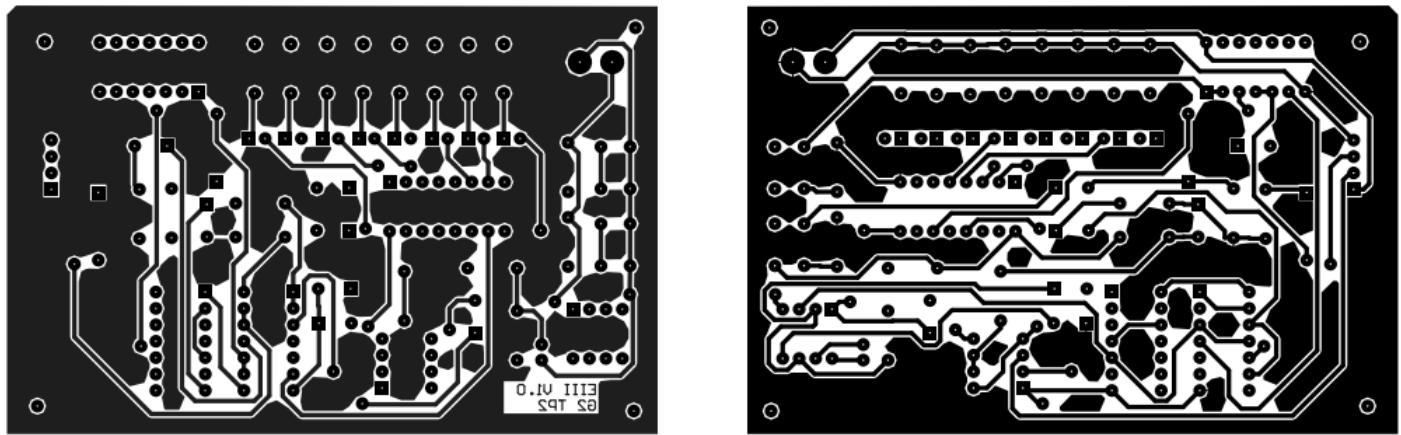
## 1.4 PCB Fabrication

To fabricate the design explained before, we used Altium 18 to create the schematic and design the PCB. Because of the amount of things taken into account explained before, we decided to implement a double layer PCB, to make this solution fit in an respectable size. Using the default library provided by Altium and the LIBEBAL library, we created the design shown on Figure 9



## TOP LAYER

## BOTTOM LAYER

Figure 9: PCB Design

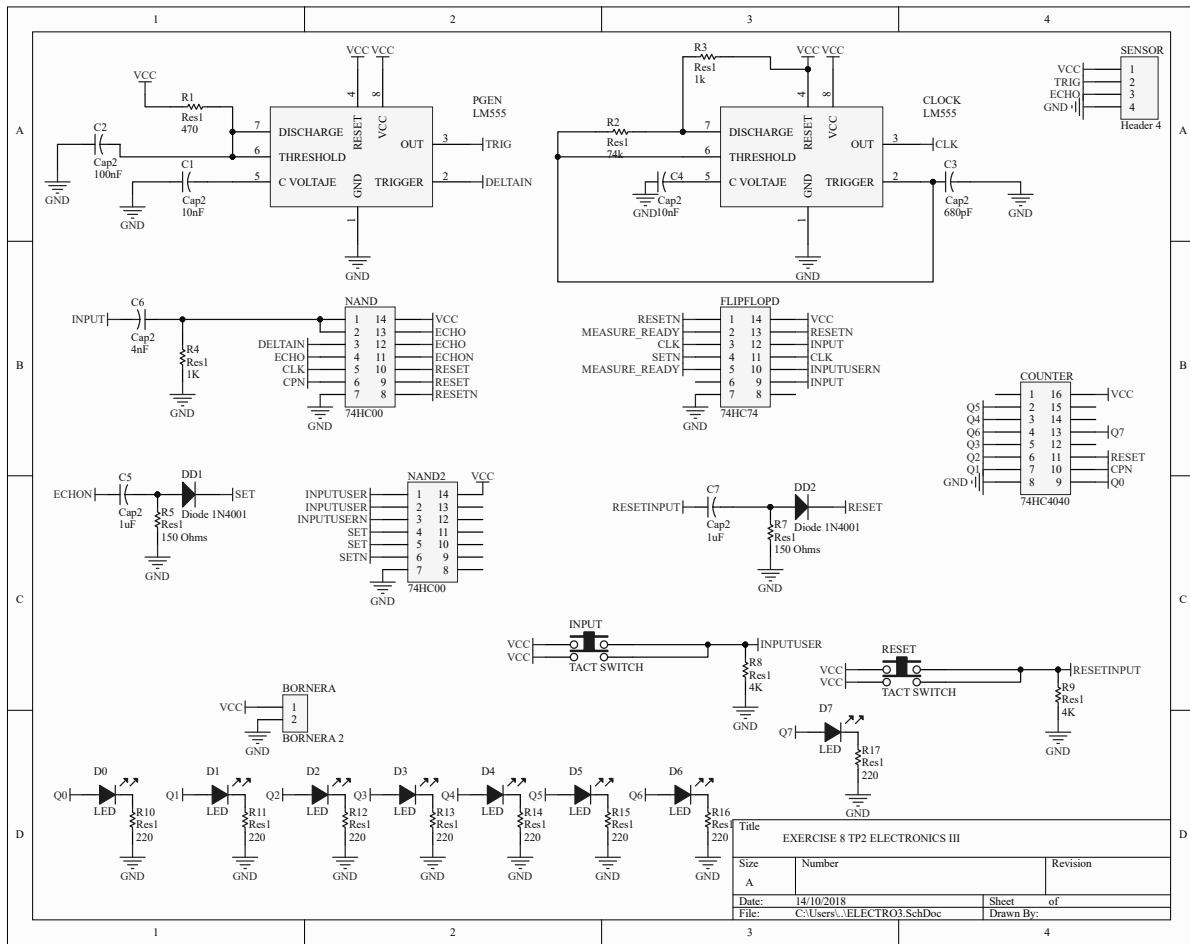


Figure 10: PCB Schematic

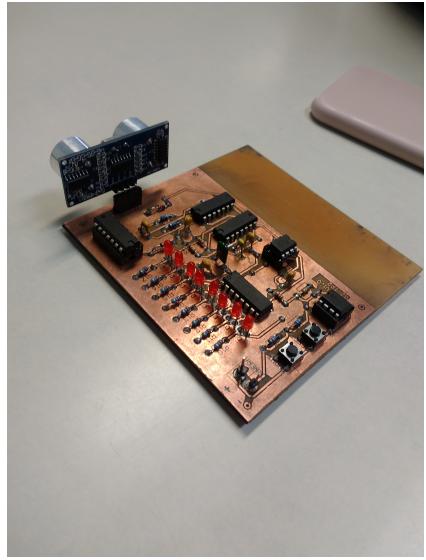


Figure 11: PCB Top Layer

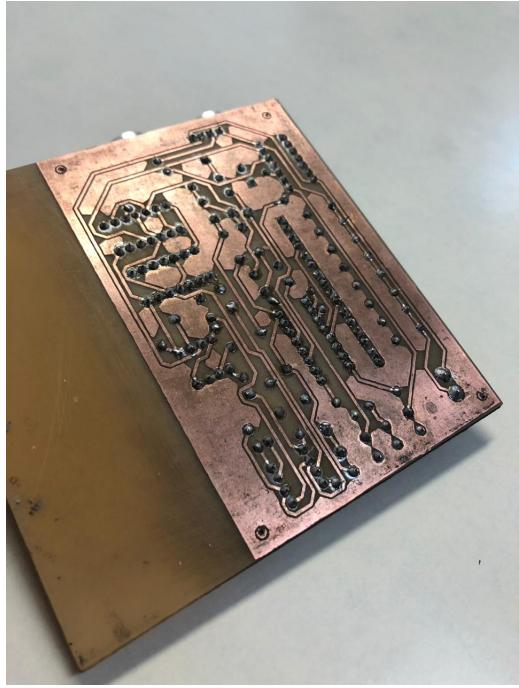


Figure 12: PCB Bottom Layer

## 1.5 Ussage

To use this solution one simply has to connect the Board to 5V voltage tension, and press the reset button. Once you are ready to measure, press the Input Button and a measurement in binary code will be displayed in the LEDs placed in the PCB. If we call  $n$  the number in decimal obtained by the LEDs, we obtain the measurement by following the next equation

$$Distance = \frac{n.80}{58} (cm)$$

Where the 80 comes from the clock speed and the 58 from the formula giver from the sensor.

## 1.6 Conclusions

We conclude that the Board behaves as expected, and by adjusting the formula with 80, we can obtain a relatively great measurement of the distance. Because fabrication and design limitations, we decided not to add the measure ready LED to display that. This was because to human perspective, the measurement is practically instant and adding 2 more components to the PCB was not enough gain to make the trouble. However, the Board to our perspective works perfectly.