

1 Implementation of Synchronous and Asynchronous 3-bit counters