

0.1 Exercise 4: Behaviour Analysis of Circuits Including a 74HC02 Gate

The 74HC02 is an integrated circuit of NOR gates.

Propagation and Transition Time' Measurements

	No-load	Circuit
t_{pHL}		
t_{pLH}		
t_f		
t_r		

Circuit's Response to Frequency Increment

Alimentation Voltage and Temperature of the IC